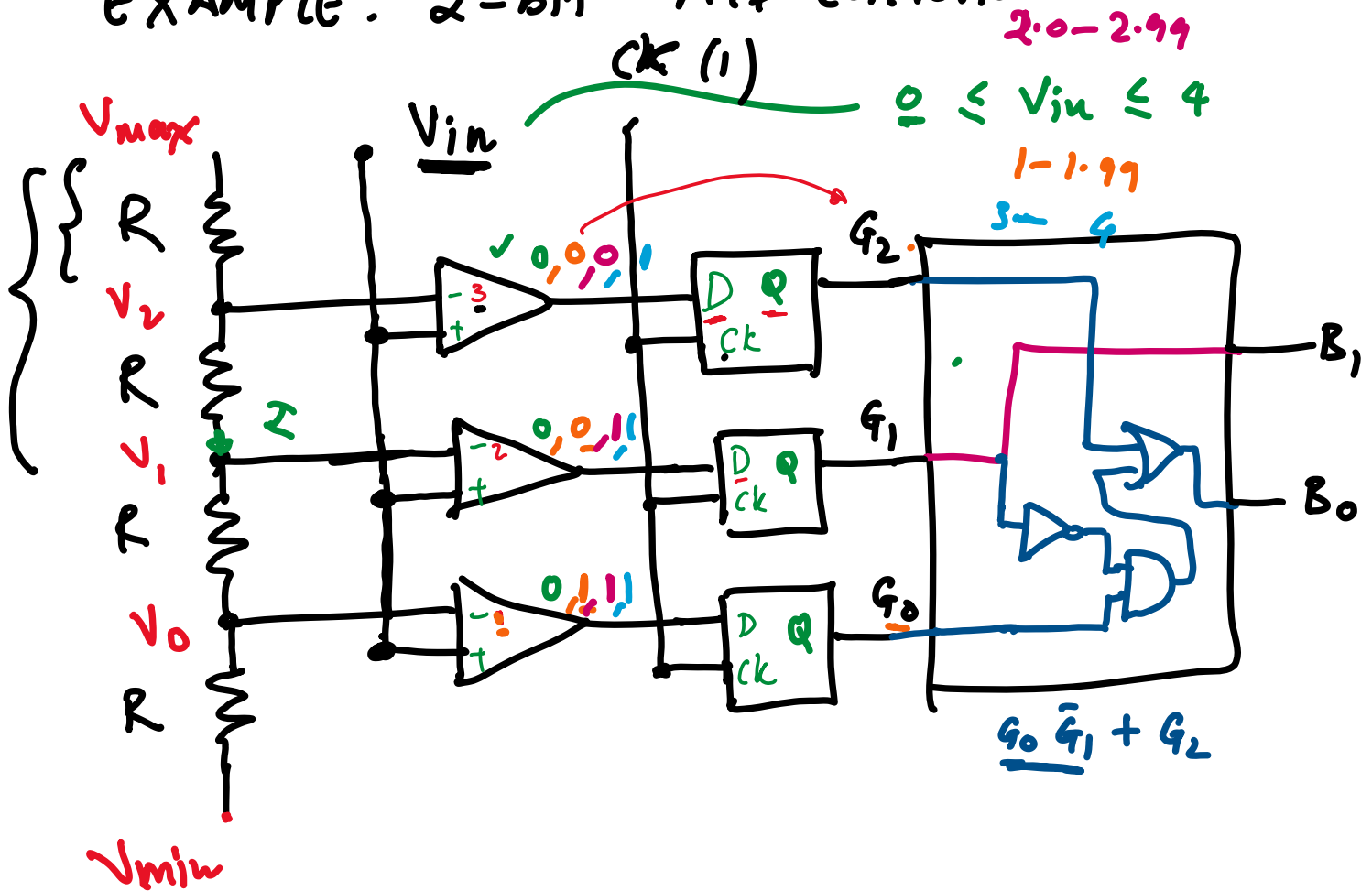


# Flash Converter (A/D)

EXAMPLE: 2-bit A/D converter



$V_{max}$ ,  $V_{min}$  are controlled by the designer  
 These are set in advance.  $V_{in} \rightarrow$  input

$$\frac{V_{max} - V_{min}}{V_{max} - V_2} = \frac{I(4R)}{I R} \Rightarrow V_{max} - V_2 = \frac{V_{max} - V_{min}}{4}$$

$$\Rightarrow V_2 = V_{max} - \frac{1}{4} \Delta V \quad (\Delta V = V_{max} - V_{min})$$

$$\left\{ \begin{array}{l} V_2 = V_{\max} - \frac{\Delta V}{4} ; V_1 = V_{\max} - \frac{\Delta V}{2} \\ V_0 = V_{\max} - \frac{3}{4} \Delta V \end{array} \right\} \textcircled{I}$$

Explanation on how this works.

$$V_{\max} = 4V ; V_{\min} = 0 ; \Delta V = V_{\max} - V_{\min}$$

From,  $\textcircled{I}$   $V_2 = 3V ; V_1 = 2V ; V_0 = 1V$

$\textcircled{1}$ $V_{in}$	$G_2 G_1 G_0$	$B_1 B_0$
0 - 0.99	0 0 0 (0)	0 0 (0)
1 - 1.99	0 0 1 (1)	0 1 (1)
2 - 2.99	0 1 1 (3)	1 0 (2)
3 - 4	1 1 1 (7)	1 1 (3)

sum-of-products  
products-of-sum

$\textcircled{1}$  op-amp  
comparator  
 $\oplus$   
D-FlipFlop  
 $G_0 G_1 G_2$

$\textcircled{2}$  Logic  
gate  
 $B_0 B_1$

$$\textcircled{2} B_0 = \underline{G_0} \bar{\underline{G_1}} + \underline{G_2}$$


$$B_1 = \underline{G_1}$$

## Flash Converter

- ① Requires only 1 CK to process each analog data (ADVANTAGE)
- ② It requires many more components compared to Successive approximation converter (DISADVANTAGE)

# Digital to Analog Conversion

EXAMPLE: 4-bit resistor ladder network.

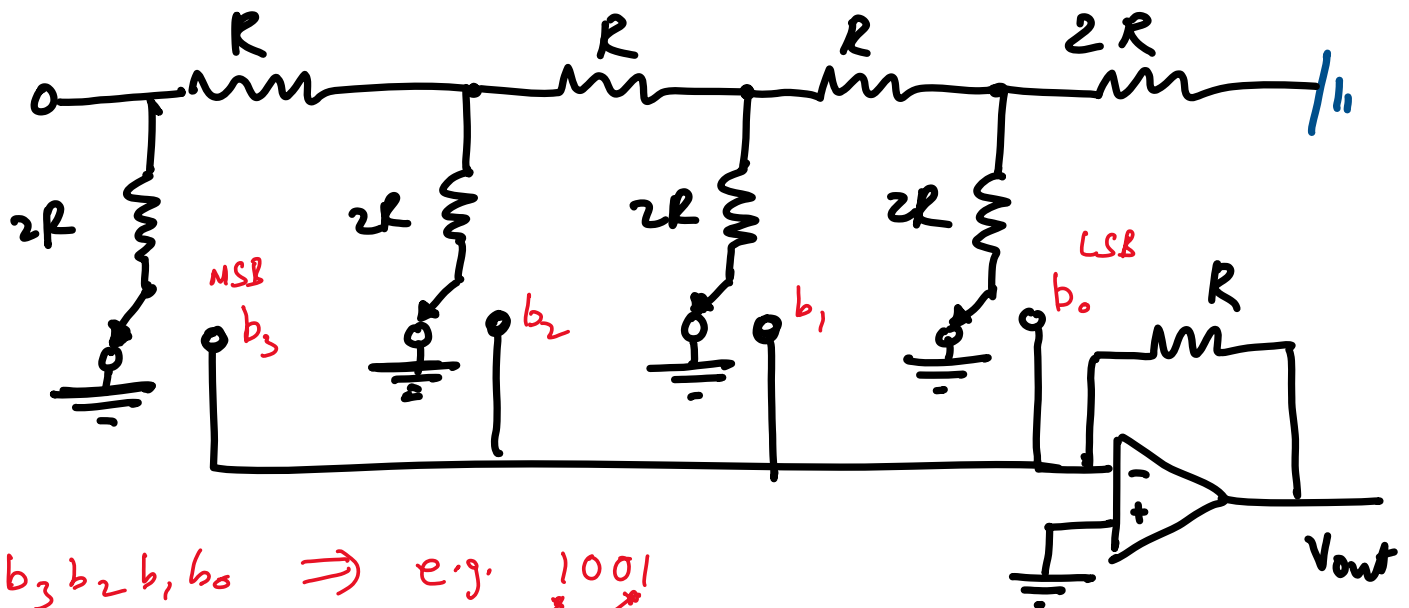


$b_3 b_2 b_1 b_0 \Rightarrow$  e.g. 1001  
 $b_3, b_0$  is closed


What we want from this circuit

- 0001  $\rightarrow$   $V_{out} = 1V$
- $b_3 b_2 b_1 b_0$
- 0010  $\rightarrow$   $V_{out} = 2V$
- $\vdots$
- 1111  $\rightarrow$   $V_{out} = 15V$

$$V_{out} = f(b_0 b_1 b_2 b_3)$$

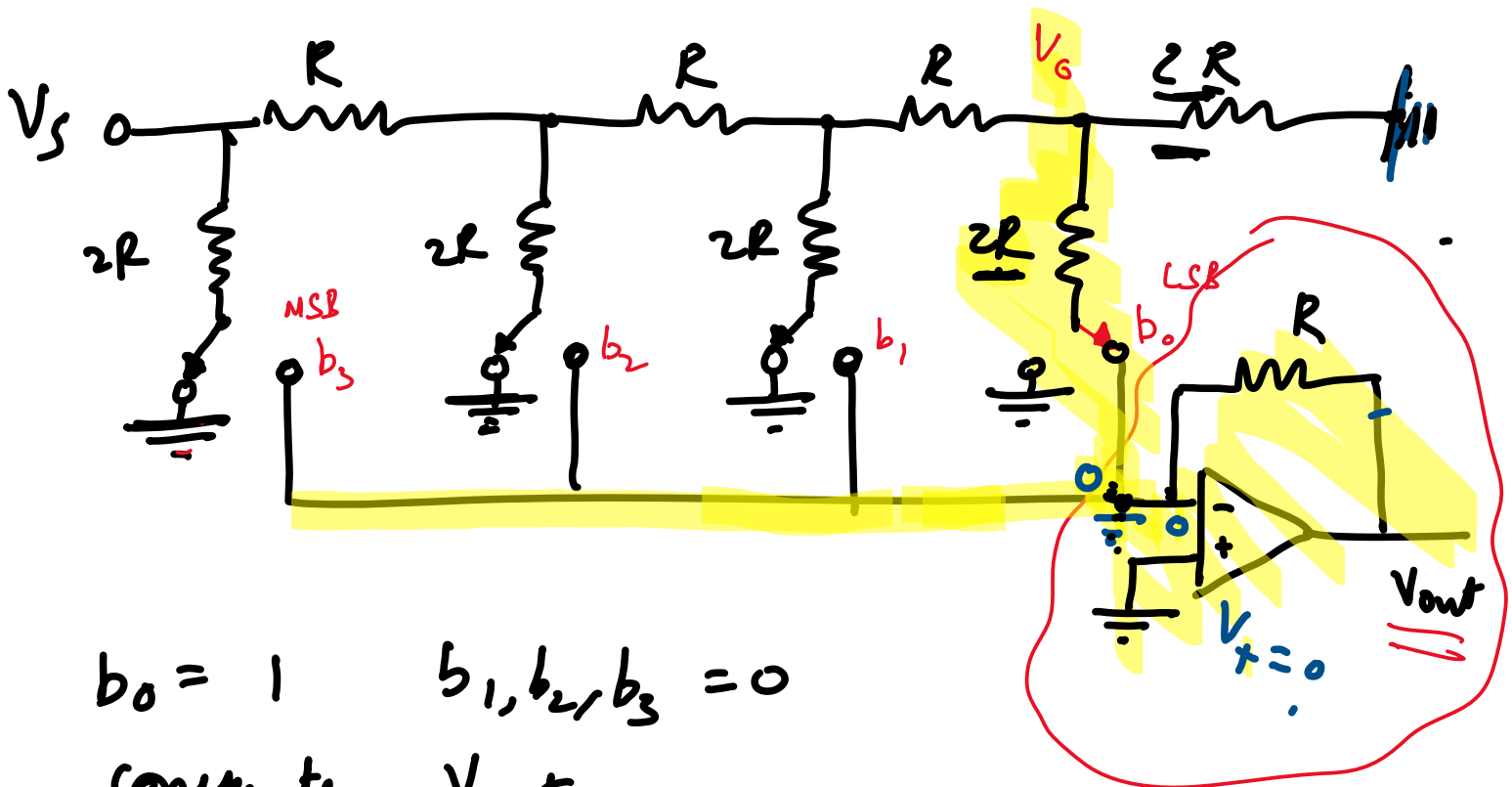

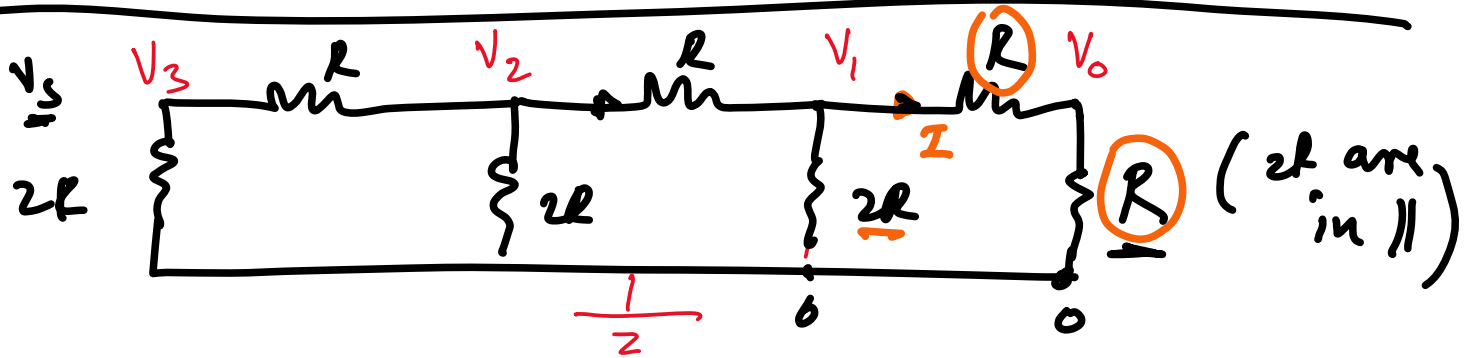$b_0 = 1 \quad b_1, b_2, b_3 = 0$   
 compute  $V_{out}$




$$\frac{V_1}{V_0} = \frac{2R I}{R I} \Rightarrow V_0 = \frac{1}{2} V_1$$

$V_1 = \frac{1}{2} V_2$  and  $V_3 = \frac{1}{2} V_2$   
 Same reasoning

$$V_0 = \frac{1}{8} V_3 = \frac{V_S}{8}$$
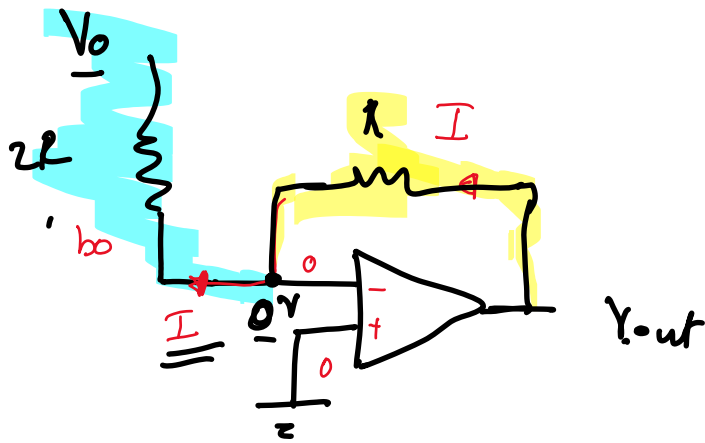
$$V_0 = \frac{1}{8} V_S \quad \leftarrow \textcircled{\text{II}}$$



$$V_{out} - 0 = IR$$

$$0 - V_0 = I(2R)$$

$$V_{out} = -\frac{1}{2} V_0$$

But  $V_0 = \frac{1}{8} V_s$

$$V_{out} = -\frac{1}{16} V_s \quad \text{--- } \textcircled{1} \quad b_0 \text{ is } (1)$$

Repeating for  $b_1 = 1$   $b_0, b_2, b_3 = 0$

$$V_{out} = -\frac{1}{8} V_s \quad - (2)$$

For  $b_2 = 1$  ;  $b_0, b_1, b_3 = 0$

$$V_{out} = -\frac{1}{4} V_s \quad - (3)$$

For  $b_3 = 1$  ;  $b_0, b_1, b_2 = 0$

$$V_{out} = -\frac{1}{2} V_s \quad - (4)$$

Combining ① - ② - ③ - ④ using  
superposition

$$V_{out} = - \left( \frac{b_3}{2} + \frac{b_2}{4} + \frac{b_1}{8} + \frac{b_0}{16} \right) V_s$$



Illustration:

Let  $V_S = 16V$ ; If  $b_0 = b_1 = b_2 = b_3 = 1$   
example input  
to the D/A  
converter

we expect  $V_{out} = 2^3 + 2^2 + 2^1 + 2^0 = 15V$   
1111 binary

Using formula

$$V_{out} = -\left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}\right) (16)$$

$$= -(8 + 4 + 2 + 1) = -15V$$